



National Semiconductor

National Temperature Sensor Handbook

Temperature Sensing Techniques

National's Temperature Sensors

Application Hints

Application Circuits

Article Reprints

Application Notes



National Semiconductor

TEMPERATURE SENSOR HANDBOOK

Kerry Lacanette

Contributors:

Emmy Denton

Robert Pease

Jerry Steele



1. INTRODUCTION TO THIS HANDBOOK.....	5
2. TEMPERATURE SENSING TECHNIQUES.....	6
<i>RTDs.....</i>	<i>6</i>
<i>Thermistors.....</i>	<i>7</i>
<i>Thermocouples.....</i>	<i>9</i>
<i>Silicon Temperature Sensors.....</i>	<i>11</i>
3. NATIONAL'S TEMPERATURE SENSOR ICS.....	12
3.1 VOLTAGE-OUTPUT ANALOG TEMPERATURE SENSORS	12
<i>LM135, LM235, LM335 Kelvin Sensors.....</i>	<i>12</i>
<i>LM35, LM45 Celsius Sensors.....</i>	<i>13</i>
<i>LM34 Fahrenheit Sensor.....</i>	<i>13</i>
<i>LM50 "Single Supply" Celsius Sensor.....</i>	<i>13</i>
<i>LM60 2.7V Single Supply Celsius Sensor.....</i>	<i>14</i>
3.2 CURRENT-OUTPUT ANALOG SENSORS	14
<i>LM134, LM234, and LM334 Current-Output Temperature Sensors.....</i>	<i>14</i>
3.3 COMPARATOR-OUTPUT TEMPERATURE SENSORS	15
<i>LM56 Low-Power Thermostat.....</i>	<i>15</i>
3.4 DIGITAL OUTPUT SENSORS	16
<i>LM75 Digital Temperature Sensor and Thermal Watchdog With Two-Wire Interface.....</i>	<i>16</i>
<i>LM78 System Monitor.....</i>	<i>17</i>
4. APPLICATION HINTS.....	19
<i>Sensor Location for Accurate Measurements.....</i>	<i>19</i>
<i>Example 1. Audio Power Amplifier.....</i>	<i>20</i>
<i>Example 2. Personal Computer.....</i>	<i>21</i>
<i>Example 3. Measuring Air Temperature.....</i>	<i>23</i>
<i>Mapping Temperature to Output Voltage or Current.....</i>	<i>24</i>
<i>Driving Capacitive Loads (These hints apply to analog-output sensors).....</i>	<i>25</i>
<i>Noise Filtering.....</i>	<i>26</i>
5. APPLICATION CIRCUITS.....	27
PERSONAL COMPUTERS	27
<i>Simple Fan Controller.....</i>	<i>27</i>
<i>Low/High Fan Controllers.....</i>	<i>28</i>
<i>Digital I/O Temperature Monitor.....</i>	<i>29</i>
INTERFACING EXTERNAL TEMPERATURE SENSORS TO PCs	30
<i>LM75-to-PC interface.....</i>	<i>30</i>
<i>Isolated LM75-to-PC.....</i>	<i>31</i>
LOW-POWER SYSTEMS	32
<i>Low-voltage, Low-Power Temperature Sensor with "Shutdown"</i>	<i>32</i>
<i>Battery Management.....</i>	<i>33</i>
<i>"No Power" Battery Temperature Monitors.....</i>	<i>34</i>
AUDIO.....	36
<i>Audio Power Amplifier Heat sink Temperature Detector and Fan Controller.....</i>	<i>36</i>
OTHER APPLICATIONS.....	37
<i>Two-Wire Temperature Sensor.....</i>	<i>37</i>
<i>4-to-20mA Current Transmitter (0°C to 100°C).....</i>	<i>39</i>
<i>Multi-Channel Temperature-to-Digital Converter.....</i>	<i>39</i>
<i>Oven Temperature Controllers.....</i>	<i>40</i>
<i>Isolated Temperature-to-Frequency Converter.....</i>	<i>41</i>



National Semiconductor



1. Introduction to This Handbook

Temperature is the most often-measured environmental quantity. This might be expected since most physical, electronic, chemical, mechanical and biological systems are affected by temperature. Some processes work well only within a narrow range of temperatures; certain chemical reactions, biological processes, and even electronic circuits perform best within limited temperature ranges. When these processes need to be optimized, control systems that keep temperature within specified limits are often used. Temperature sensors provide inputs to those control systems.

Many electronic components can be damaged by exposure to high temperatures, and some can be damaged by exposure to low temperatures. Semiconductor devices and LCDs (Liquid Crystal Displays) are examples of commonly-used components that can be damaged by temperature extremes. When temperature limits are exceeded, action must be taken to protect the system. In these systems, temperature sensing helps enhance reliability. One example of such a system is a personal computer. The computer's motherboard and hard disk drive generate a great deal of heat. The internal fan helps cool the system, but if the fan fails, or if airflow is blocked, system components could be permanently damaged. By sensing the temperature inside the computer's case, high-temperature conditions can be detected and actions can be taken to reduce system temperature, or even shut the system down to avert catastrophe.

Other applications simply require temperature data so that temperature's effect on a process may be accounted for. Examples are battery chargers (batteries' charge capacities vary with temperature and cell temperature can help determine the optimum point at which to terminate fast charging), crystal oscillators (oscillation frequency varies with temperature) and LCDs (contrast is temperature-dependent and can be compensated if the temperature is known).

This handbook provides an introduction to temperature sensing, with a focus on silicon-based sensors. Included are several example application circuits, reprints of magazine articles on temperature sensing, and a selection guide to help you choose a silicon-based sensor that is appropriate for your application.



2. Temperature Sensing Techniques

Several temperature sensing techniques are currently in widespread usage. The most common of these are RTDs, thermocouples, thermistors, and sensor ICs. The right one for your application depends on the required temperature range, linearity, accuracy, cost, features, and ease of designing the necessary support circuitry. In this section we discuss the characteristics of the most common temperature sensing techniques.

RTDs

Resistive sensors use a sensing element whose resistance varies with temperature. A platinum **RTD** (Resistance Temperature Detector) consists of a coil of platinum wire wound around a bobbin, or a film of platinum deposited on a substrate. In either case, the sensor's resistance-temperature curve is a nearly-linear function, as shown in Figure 2.1. The RTD's resistance curve is the lower one; a straight line is also shown for reference. Nonlinearity is several degrees at temperature extremes, but is highly predictable and repeatable. Correction of this nonlinearity may be done with a linearizing circuit or by digitizing the measured resistance value and using a lookup table to apply correction factors. Because of the curve's high degree of repeatability over a wide temperature range (roughly -250 degrees C to +750 degrees C), and platinum's stability (even when hot), you'll find RTDs in a variety of precision sensing applications.

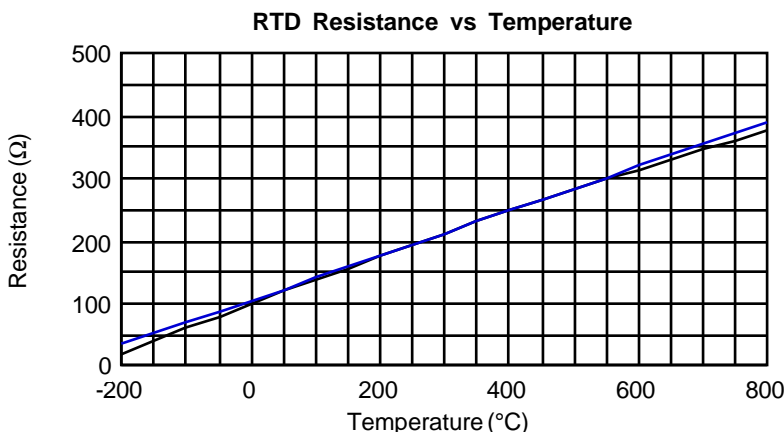


Figure 2.1. RTD Resistance vs. Temperature. The upper curve is a straight line for reference.

Complexity of RTD signal processing circuitry varies substantially depending on the application. Usually, a known, accurate current is forced through the sensor, and the voltage across the sensor is measured. Several components, each of which generates its own errors, are necessary. When leads to the sensor are long, four-wire connections to the sensor can eliminate the effects of lead resistance, but this may increase the amplifier's complexity.




Low-voltage operation is possible with resistive sensors -- there are no inherent minimum voltage limitations on these devices -- and there are enough precision low-voltage amplifiers available to make low voltage operation reasonable to achieve. Low-power operation is a little tougher, but it can be done at the expense of complexity by using intermittent power techniques. By energizing the sensor only when a measurement needs to be made, power consumption can be minimized.

RTDs have drawbacks in some applications. For example, the cost of a wire-wound platinum RTD tends to be relatively high. On the other hand, thin-film RTDs and sensors made from other metals can cost as little as a few dollars. Also, self-heating can occur in these devices. The power required to energize the sensor raises its temperature, which affects measurement accuracy. Circuits that drive the sensor with a few mA of current can develop self-heating errors of several degrees. The nonlinearity of the resistance-vs.-temperature curve is a disadvantage in some applications, but as mentioned above, it is very predictable and therefore correctable.


Thermistors

Another type of resistive sensor is the thermistor. Low-cost thermistors often perform simple measurement or trip-point detection functions in low-cost systems. Low-precision thermistors are very inexpensive; at higher price points, they can be selected for better precision at a single temperature. A thermistor's resistance-temperature function is very nonlinear (Figure 2.2), so if you want to measure a wide range of temperatures, you'll find it necessary to perform substantial linearization. An alternative is to purchase linearized devices, which generally consist of an array of two thermistors with some fixed resistors. These are much more expensive and less sensitive than single thermistors, but their accuracy can be excellent.

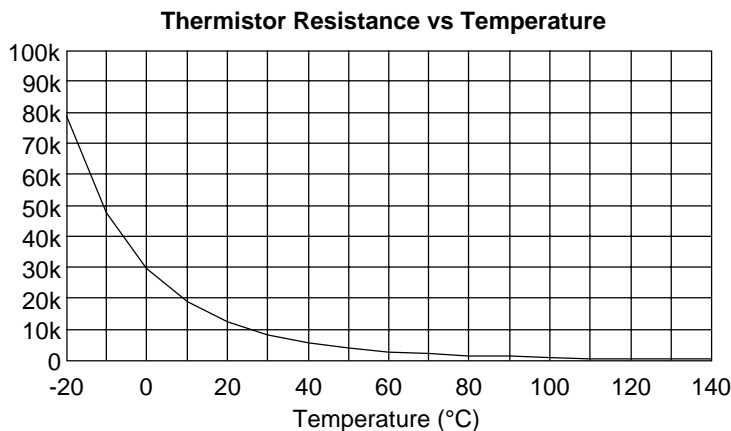Simple thermistor-based set-point thermostat or controller applications can be implemented with very few components - just the thermistor, a comparator, and a few resistors will do the job.



(a)

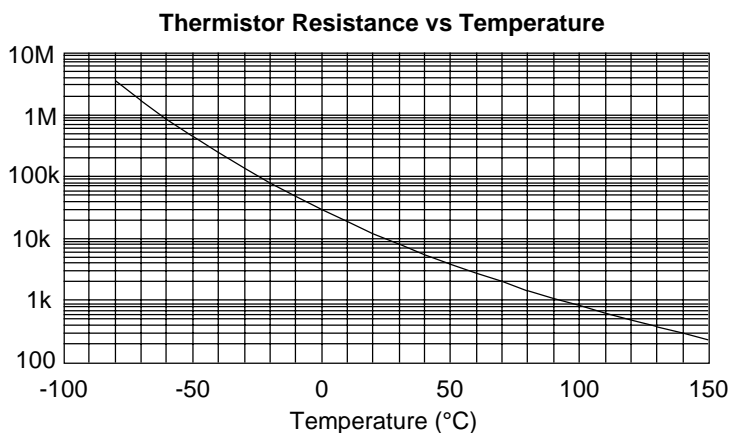


(b)

Figure 2.2. Thermistor Resistance vs. Temperature. (a) linear scale. (b) logarithmic scale.

When functionality requirements are more involved (for example if multiple trip points or analog-to-digital conversion are necessary), external circuitry and cost increase quickly. Consequently, you'll typically use low-cost thermistors only in applications with minimal functionality requirements. Thermistors can be affected by self-heating, usually at higher temperatures where their resistances are lower. As with RTDs, there are no fundamental reasons why thermistors shouldn't be used on low supply voltages. External active components such as comparators or amplifiers will usually limit the low end of the supply voltage range. You can find thermistors that will work over a temperature range from about -100°C to +550°C although most are rated for maximum operating temperatures from 100°C to 150°C.




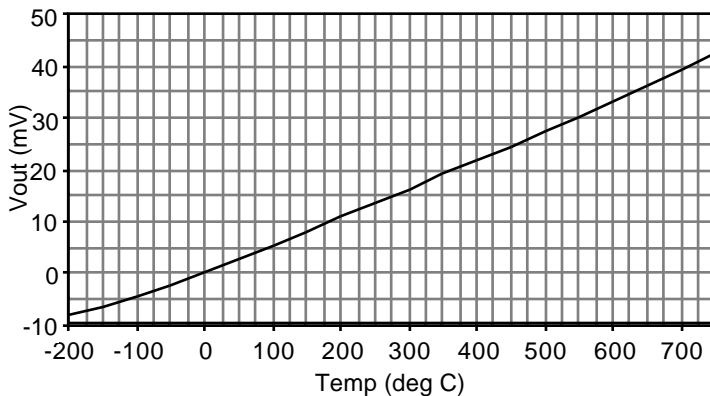Type J Thermocouple Output Voltage vs Temperature



(a)

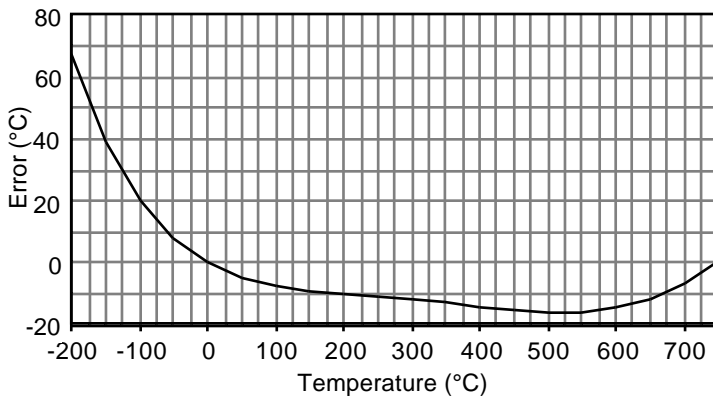Type J Thermocouple Deviation From Straight Line



(b)

Figure 2.4. (a) Output voltage as a function of temperature for a Type J thermocouple. (b) Approximate error in °C vs. a straight line that passes through the curve at 0°C and 750°C



Table 1. Seebeck Coefficients and Temperature Ranges for various thermocouple types.

Type	Seebeck Coefficient $\mu\text{V}/^\circ\text{C}$	Temperature Range ($^\circ\text{C}$)
E	58.5@0 $^\circ\text{C}$	0 to 1700
J	50.2@0 $^\circ\text{C}$	-0 to 750
K	39.4@0 $^\circ\text{C}$	-200 to 1250
R	11.5@0 $^\circ\text{C}$	0 to 1450

Silicon Temperature Sensors

Integrated circuit temperature sensors differ significantly from the other types in a couple of important ways. The first is operating temperature range. A temperature sensor IC can operate over the nominal IC temperature range of -55 $^\circ\text{C}$ to +150 $^\circ\text{C}$. Some devices go beyond this range, while others, because of package or cost constraints, operate over a narrower range. The second major difference is functionality. A silicon temperature sensor is an integrated circuit, and can therefore include extensive signal processing circuitry within the same package as the sensor. You don't need to design cold-junction compensation or linearization circuits for temperature sensor ICs, and unless you have extremely specialized system requirements, there is no need to design comparator or ADC circuits to convert their analog outputs to logic levels or digital codes. Those functions are already built into several commercial ICs.



3. National's Temperature Sensor ICs

National builds a wide variety of temperature sensor ICs that are intended to simplify the broadest possible range of temperature sensing challenges. Some of these are analog circuits, with either voltage or current output. Others combine analog sensing circuits with voltage comparators to provide "thermostat" or "alarm" functions. Still other sensor ICs combine analog sensing circuitry with digital I/O and control registers, making them an ideal solution for microprocessor-based systems such as personal computers.

Below is a summary of National's sensor products as of August, 1996. Unless otherwise noted, the specifications listed in this section are the guaranteed limits for the best grade device.

3.1 Voltage-Output Analog Temperature Sensors

LM135, LM235, LM335 Kelvin Sensors

The LM135, LM235, and LM335 develop an output voltage proportional to absolute temperature with a nominal temperature coefficient of 10mV/K. The nominal output voltage is therefore 2.73V at 0°C, and 3.73V at 100°C. The sensors in this family operate like 2-terminal shunt voltage references, and are nominally connected as shown in Figure 3.1. The third terminal allows you to adjust accuracy using a trimpot as shown in the Figure. The error of an untrimmed LM135A over the full -55°C to +150°C range is less than $\pm 2.7^\circ\text{C}$. Using an external trimpot to adjust accuracy reduces error to less than $\pm 1^\circ\text{C}$ over the same temperature range. The sensors in this family are available in the plastic TO-92 and SO-8 packages, and in the TO-46 metal can.

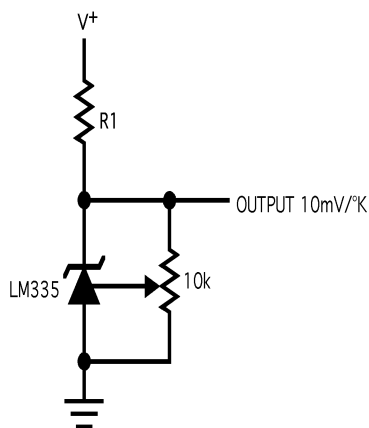


Figure 3.1. Typical Connection for LM135, LM235, and LM335. Adjust the potentiometer for the correct output voltage at a known temperature (for example 2.982V @ 25°C), to obtain better than $\pm 1^\circ\text{C}$ accuracy over the -55°C to +150°C temperature range.



LM35, LM45 Celsius Sensors

The LM35 and LM45 are three-terminal devices that produce output voltages proportional to °C (10mV/°C), so the nominal output voltage is 250mV at 25°C and 1.000V at 100°C. These sensors can measure temperatures below 0°C by using a pull-down resistor from the output pin to a voltage below the “ground” pin (see the “Applications Hints” section). The LM35 is more accurate ($\pm 1^\circ\text{C}$ from -55°C to $+150^\circ\text{C}$ vs. $\pm 3^\circ\text{C}$ from -20°C to $+100^\circ\text{C}$), while the LM45 is available in the “Tiny” SOT-23 package. The LM35 is available in the plastic TO-92 and SO-8 packages, and in the TO-46 metal can.

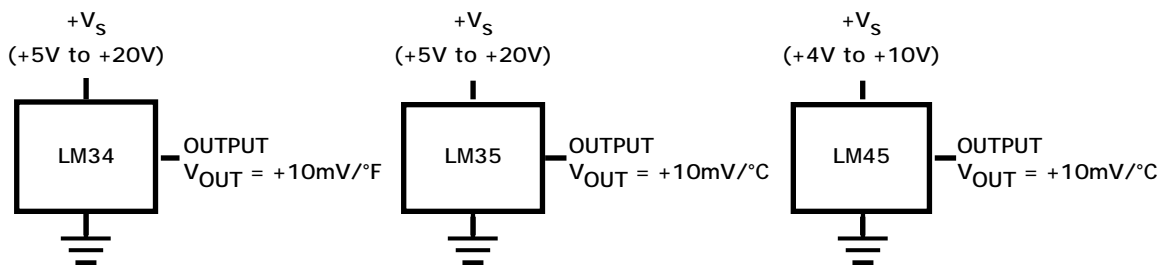


Figure 3.2. LM35, 45, 34 Typical Connections. Each IC is essentially a 3-terminal device (supply, ground, and output), although some are available in packages with more pins.

LM34 Fahrenheit Sensor

The LM34 is similar to the LM35, but its output voltage is proportional to °F (10mV/°F). Its accuracy is similar to the LM35 ($\pm 2^\circ\text{F}$ from -50°F to $+300^\circ\text{F}$), and it is available in the same TO-92, SO-8, and TO-46 packages as the LM35.

LM50 “Single Supply” Celsius Sensor

The LM50 is called a “Single Supply” Celsius Sensor because, unlike the LM35 and LM45, it can measure negative temperatures without taking its output pin below its ground pin (see the “Applications Hints” section). This can simplify external circuitry in some applications. The LM50’s output voltage has a 10mV/°C slope, and a 500mV “offset”. Thus, the output voltage is 500mV at 0°C, 100mV at -40°C , and 1.5V at $+100^\circ\text{C}$. Accuracy is within 3°C over the full -40°C to $+125^\circ\text{C}$ operating temperature range. The LM50 is available in the SOT-23 package.

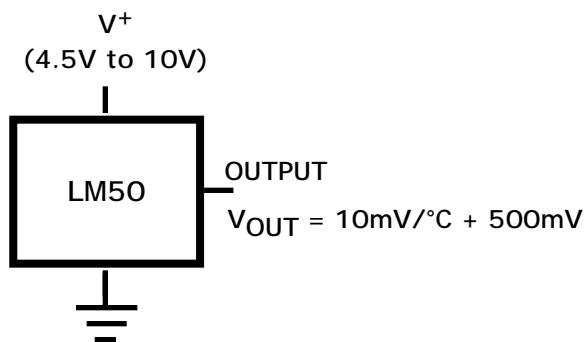


Figure 3.3. LM50 Typical Connection

LM60 2.7V Single Supply Celsius Sensor

The LM60 is similar to the LM50, but is intended for use in applications with supply voltages as low as 2.7V. Its 110 μ A supply current drain is low enough to make the LM60 an ideal sensor for battery-powered systems. The LM60's output voltage has a 6.25mV/ $^{\circ}$ C slope, and a 424mV "offset". This results in output voltages of 424mV at 0 $^{\circ}$ C, 174mV at -40 $^{\circ}$ C, and 1.049V at 100 $^{\circ}$ C. The LM60 is available in the SOT-23 package.

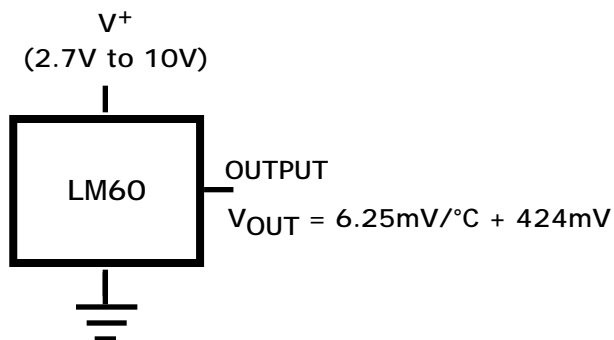


Figure 3.4. LM60 Typical Connection

3.2 Current-Output Analog Sensors

LM134, LM234, and LM334 Current-Output Temperature Sensors

Although its data sheet calls it an "adjustable current source", the LM134 is also a current-output temperature sensor with an output current proportional to absolute temperature. The sensitivity is set using a single external resistor. Typical sensitivities are in the .1 μ A/ $^{\circ}$ C to 3 μ A/ $^{\circ}$ C range, with 1 μ A/ $^{\circ}$ C being a good nominal value. By adjusting the value of the external resistor, the sensitivity can be trimmed for good accuracy over the full operating temperature



range (-55°C to +125°C for the LM134, -25°C to +100°C for the LM234, and 0°C to +70°C for the LM334). The LM134 typically needs only 1.2V supply voltage, so it can be useful in applications with very limited voltage headroom. Devices in this family are available in SO-8 and TO-92 plastic packages and TO-46 metal cans.

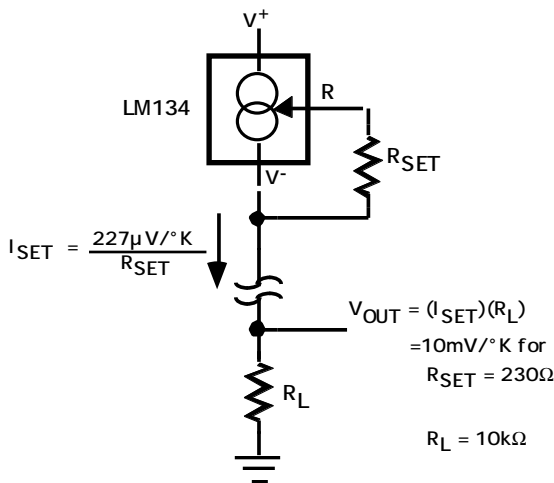


Figure 3.5. LM134 Typical Connection. R_{SET} controls the ratio of output current to temperature.

3.3 Comparator-Output Temperature Sensors

LM56 Low-Power Thermostat

The LM56 includes a temperature sensor (similar to the LM60), a 1.25V voltage reference, and two comparators with preset hysteresis. It will operate from power supply voltages between 2.7V and 10V, and draws a maximum of 200μA from the power supply. The operating temperature range is -40°C to +125°C. Comparator trip point tolerance, including all sensor, reference, and comparator errors (but not including external resistor errors) is 2°C from 25°C to 85°C, and 3°C from -40°C to +125°C.

The internal temperature sensor develops an output voltage of 6.2mV x T(°C) + 395mV. Three external resistors set the thresholds for the two comparators.

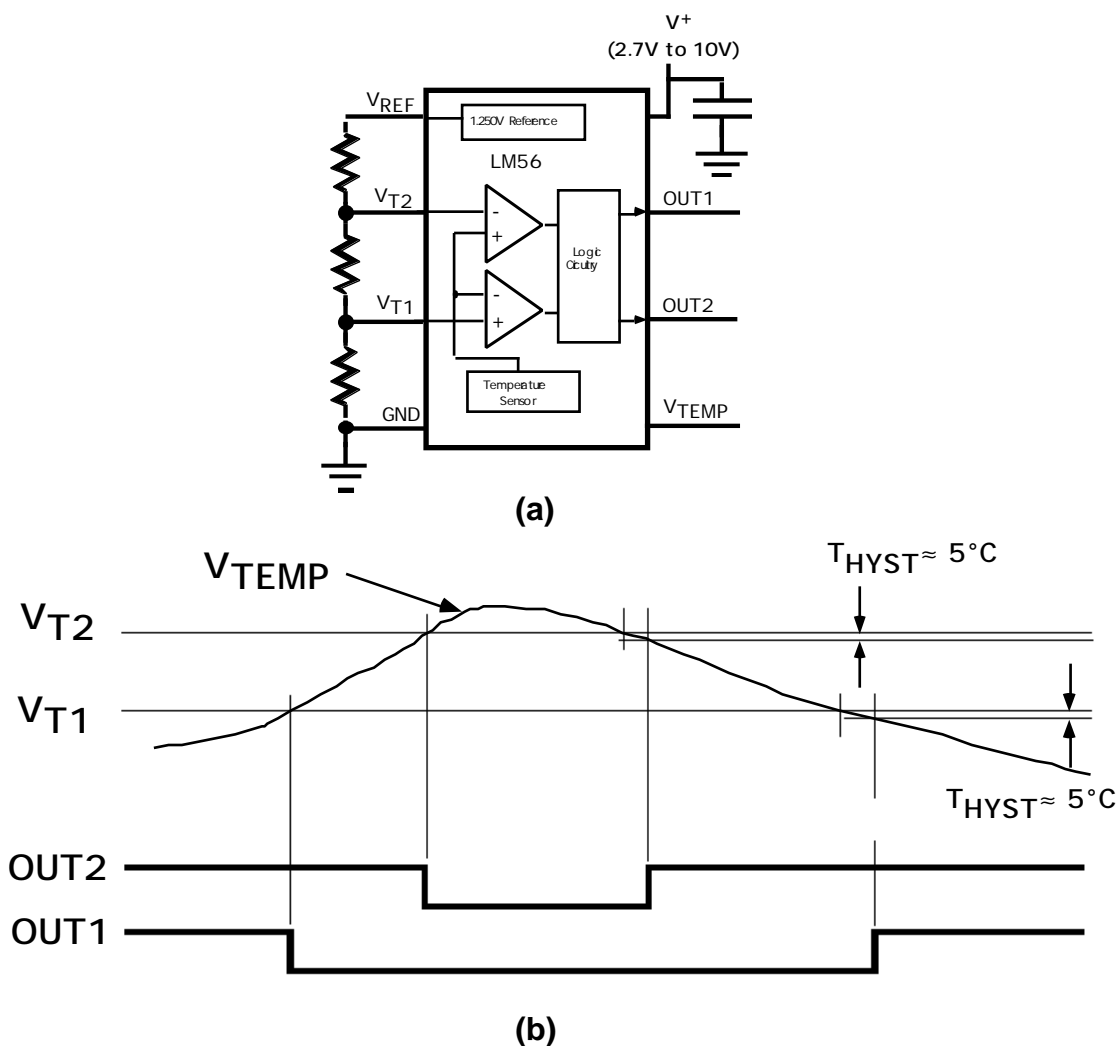


Figure 3.6. (a) LM56 block diagram. (b) Comparator outputs as a function of temperature.

3.4 Digital Output Sensors

LM75 Digital Temperature Sensor and Thermal Watchdog With Two-Wire Interface

The LM75 contains a temperature sensor, a delta-sigma analog-to-digital converter (ADC), a two-wire digital interface, and registers for controlling the IC's operation. The two-wire interface follows the I²C[®] protocol. Temperature is continuously being measured, and can be read at any time. If desired, the host processor can instruct the LM75 to monitor temperature and take an output pin



high or low (the sign is programmable) if temperature exceeds a programmed limit. A second, lower threshold temperature can also be programmed, and the host can be notified when temperature has dropped below this threshold. Thus, the LM75 is the heart of a temperature monitoring and control subsystem for microprocessor-based systems such as personal computers. Temperature data is represented by a 9-bit word (1 sign bit and 8 magnitude bits), resulting in 0.5°C resolution. Accuracy is $\pm 2^\circ\text{C}$ from -25°C to $+100^\circ\text{C}$ and $\pm 3^\circ\text{C}$ from -55°C to $+125^\circ\text{C}$. The LM75 is available in an 8-pin SO package.

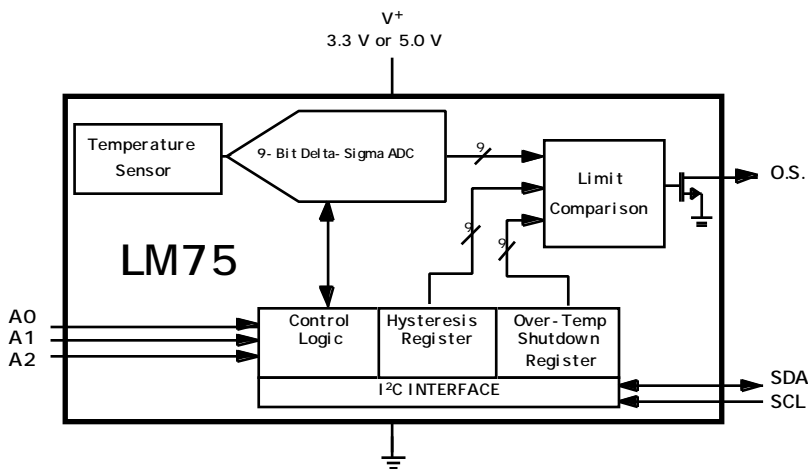


Figure 3.7. LM75 Block Diagram.

LM78 System Monitor

The LM78 is a highly-integrated Data Acquisition system IC that can monitor several kinds of analog inputs simultaneously, including temperature, frequency, and analog voltage. It is an ideal single-chip solution for improving the reliability of servers, Personal Computers, or virtually any microprocessor-based instrument or system. The IC includes a temperature sensor, I²C and ISA interfaces, a multiple-input 8-bit ADC (five positive inputs and 2 negative inputs), fan speed counters, several control and memory registers, and numerous other functions. In a PC, the LM78 can be used to monitor power supply voltages, temperatures, and fan speeds. The values of these analog quantities are continuously digitized and can be read at any time. Programmable WATCHDOG™ limits for any of these analog quantities activate a fully-programmable and maskable interrupt system with two outputs. An input is provided for the overtemperature outputs of additional temperature sensors (such as the LM56 and LM75) and this is linked to the interrupt system. Additional inputs are provided for Chassis Intrusion detection circuits, VID monitor inputs, and chainable interrupt. A 32-byte auto-increment RAM is provided for POST (Power On Self Test) code storage.



The LM78 operates from a single 5V power supply and draws less than 1mA of supply current while operating. In shutdown mode, supply current drops to 10 μ A.

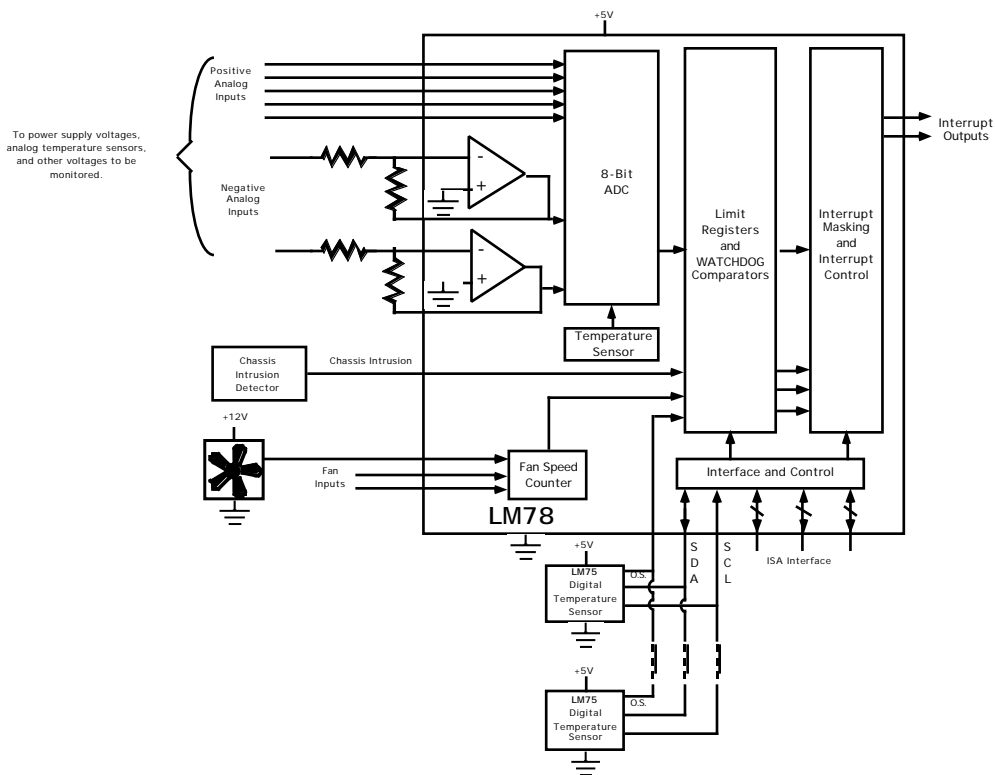


Figure 3.8. The LM78 is a highly-integrated system monitoring circuit that tracks not only temperature, but also power supply voltages, fan speed, and other analog quantities.



4. Application Hints

The following Application Hints apply to most of National's temperature sensor ICs. For hints that are specific to a particular sensor, please refer to that sensor's data sheet.

Sensor Location for Accurate Measurements

A temperature sensor produces an output, whether analog or digital, that depends on the temperature of the sensor. Heat is conducted to the sensing element through the sensor's package and its metal leads. In general, a sensor in a metal package (such as an LM35 in a TO46) will have a dominant thermal path through the package. For sensors in plastic packages like TO-92, SO-8, and SOT-23, the leads provide the dominant thermal path. Therefore, a board-mounted IC sensor will do a fine job of measuring the temperature of the circuit board (especially the traces to which the leads are soldered). If the board's temperature is very close to the ambient air temperature (that is, if the board has no significant heat generators mounted on it), the sensor's temperature will also be very near that of the ambient air.

If you want to measure the temperature of something other than the circuit board, you must ensure that the sensor and its leads are at the same temperature as the object you wish to measure. This usually involves making a good mechanical and thermal contact by, for example, attaching the sensor (and its leads) to the object being measured with thermally-conductive epoxy. If electrical connections can be made directly from the sensor's leads to the object being measured, soldering the leads of an IC sensor to the object will give a good thermal connection. If the ambient air temperature is the same as that of the surface being measured, the sensor will be within a fraction of a degree of the surface temperature. If the air temperature is much higher or lower than the surface temperature, the temperature of the sensor die will be at an intermediate temperature between the surface temperature and the air temperature. A sensor in a plastic package (a TO-92 or SOT-23, for example) will indicate a temperature very close to that of its leads (which will be very close to the circuit board's temperature), with air temperature having a less significant effect. A sensor in a metal package (like a TO-46) will usually be influenced more by air temperature. The influence of air temperature can be further increased by gluing or clamping a heat sink to the metal package.

If liquid temperature is to be measured, a sensor can be mounted inside a sealed-end metal tube, and can then be dipped into a bath or screwed into a threaded hole in a tank. Temperature sensors and any accompanying wiring and circuits must be kept insulated and dry, to avoid leakage and corrosion. This is especially



true for IC temperature sensors if the circuit may operate at cold temperatures where condensation can occur. Printed-circuit coatings and varnishes such as Humiseal and epoxy paints or dips are often used to ensure that moisture cannot corrode the sensor or its connections.

So where should you put the sensor in your application? Here are three examples:

Example 1. Audio Power Amplifier

It is often desirable to measure temperature in an audio power amplifier to protect the electronics from overheating, either by activating a cooling fan or shutting the system down. Even an IC amplifier that contains internal circuitry to shut the amplifier down in the event of overheating (National's Overture-series amplifiers, for example) can benefit from additional temperature sensing. By activating a cooling fan when temperature gets high, the system can produce more output power for longer periods of time, but still avoids having the fan (and producing noise) when output levels are low.

Audio amplifiers that dissipate more than a few watts virtually always have their power devices (either discrete transistors or an entire monolithic amplifier) bolted to a heat sink. The heat sink's temperature depends on ambient temperature, the power device's case temperature, the power device's power dissipation, and the thermal resistance from the case to the heat sink. Similarly, the power device's case temperature depends on the device's power dissipation and the thermal resistance from the silicon to the case. The heat sink's temperature is therefore not equal to the "junction temperature", but it is dependent on it and related to it.

A practical way to monitor the power device's temperature is to mount the sensor on the heat sink. The sensor's temperature will be lower than that of the power device's die, but if you understand the correlation between heat sink temperature and die temperature, the sensor's output will still be useful.

Figure 4.1 shows an example of a monolithic power amplifier bolted to a heat sink. Next to the amplifier is a temperature sensor IC in a TO-46 metal can package. The sensor package is in a hole drilled into the heat sink; the sensor is cemented to the heat sink with heat-conducting epoxy. Heat is conducted from the heat sink through the sensor's case, and from the circuit board through the sensor's leads. Depending on the amplifier, the heat sink, the printed circuit board layout, and the sensor, the best indication of the amplifier's temperature may be obtained through the metal package or through the sensor's leads.



National Semiconductor

The amplifier IC's leads will normally be within a few degrees of the temperature of the heat sink near the amplifier. If the amplifier is soldered directly to the printed circuit board, and if the leads are short, the circuit board traces at the amplifier's leads will be quite close to the heat sink temperature -- sometimes higher, sometimes lower, depending on the thermal characteristics of the system. Therefore, if the sensor can be soldered to a point very close to the amplifier's leads, you'll get a good correlation with heat sink temperature. This is especially good news if you're using a temperature sensor in a plastic package, since thermal conduction for such a device is through the leads. Locate the sensor as close as possible to the amplifier's leads. If the amplifier has a ground pin, place the sensor's ground pin right next to that of the amplifier and try to keep the other sensor leads at the same temperature as the amplifier's leads.

If the heat sink is mounted to the back side of the printed circuit board, the sensor can be mounted on the top of the board, as close as practical to the power device(s). This will provide good correlation between measured temperature and heat sink temperature.

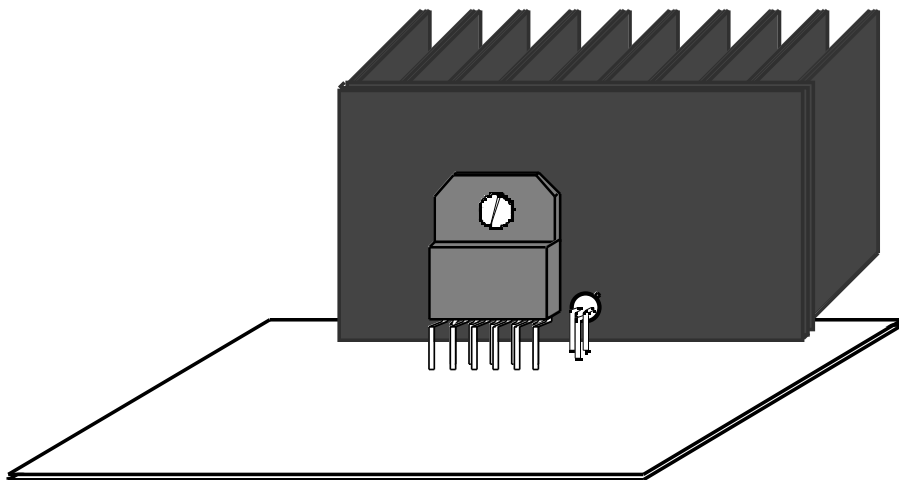


Figure 4.1. TO-220 power amplifier and TO-46 sensor mounted on heat sink. Excellent results can also be obtained by locating the sensor on the circuit board very close to the amplifier IC's leads.

Example 2. Personal Computer

High-performance microprocessors such as the Pentium or Power PC families consume a lot of power and can get hot enough to suffer catastrophic damage due to excessive temperature. To enhance system reliability, it is often desirable



to monitor processor temperature and activate a cooling fan, slow down the system clock, or shut the system down completely if the processor gets too hot.

As with power amplifiers, there are several potential mounting sites for the sensor. One such location is in the center of a hole drilled into the microprocessor's heat sink, shown as location "a" in Figure 4.2. The heat sink, which can be clipped to the processor or attached with epoxy, generally sits on top of the processor. The advantage of this location is that the sensor's temperature will be within a few degrees of the microprocessor's case temperature in a typical assembly. A disadvantage is that relatively long leads will be required to return the processor's output to the circuit board. Another disadvantage is that if the heat-sink-to-microprocessor thermal connection degrades (either because of bad epoxy or because a clip-on heat sink gets "bumped" and is no longer in intimate contact with the processor), the sensor-to-microprocessor connection will probably also be disrupted, which means that the sensor will be at a lower than normal temperature while the processor temperature is rising to a potentially damaging level.

Another potential location is in the cavity beneath a socketed processor (Figure 4.2, location "b"). An advantage of this site is that, since the sensor is attached to the circuit board using conventional surface-mounting techniques, assembly is straightforward. Another advantage is that the sensor is isolated from air flow and will not be influenced excessively by changes in ambient temperature, fan speed, or direction of cooling air flow. Also, if the heat sink becomes detached from the microprocessor, the sensor will indicate an increase in microprocessor temperature. A disadvantage is that the thermal contact between the sensor and the processor is not as good as in the previous example, which can result in temperature differences between the sensor and the microprocessor case of 5°C to 10°C. This is only a minor disadvantage, however, and this approach is the most practical one in many systems.

It is also possible to mount the sensor on the circuit board next to the microprocessor's socket (location "c"). This is another technique that is compatible with large-volume manufacturing, but the correlation between sensor temperature and processor temperature is much weaker (the microprocessor case can be as much as 20°C warmer than the sensor).

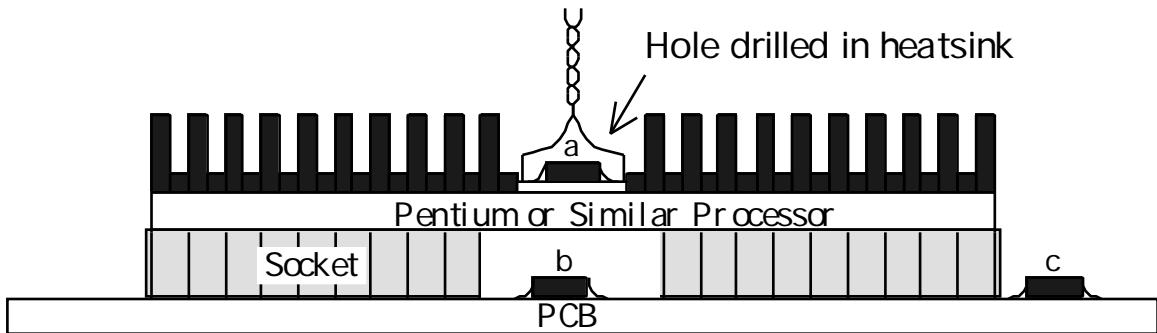


Figure 4.2. Three potential sensor locations for high-performance processor monitoring.

Finally, in some lower-cost systems the microprocessor may be soldered to the motherboard, with the heat sink mounted on the opposite side of the motherboard, as shown in Figure 4.3. In these systems, the sensor can be soldered to the board at the edge of the heat sink. Since the microprocessor is in close contact with the motherboard, the sensor's temperature will be closer to that of the microprocessor than for a socketed microprocessor.

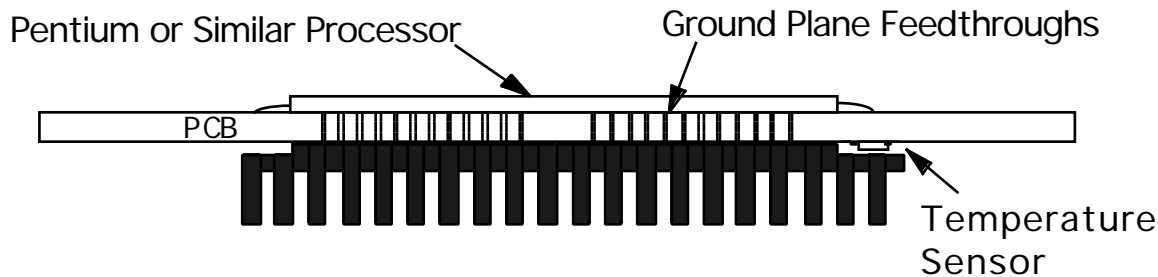


Figure 4.3. Sensor mounted near edge of soldered processor.

Example 3. Measuring Air Temperature

Because the sensor's leads are often the dominant thermal path, a board-mounted sensor will usually do an excellent job of measuring board temperature. But what if you want to measure air temperature? If the board is at the same temperature as the air, you're in luck.

If the board and the air are at different temperatures, things get more complicated. The sensor can be isolated from the board using long leads. If the sensor is in a metal can, a clip-on heat sink can bring the sensor's temperature close to ambient. If the sensor is in a plastic package, it may need to be mounted on a small "sub-board", which can then be thermally isolated from the main board with long leads.



For more information on finding the ideal location for a temperature sensor, refer to the article “Get Maximum Accuracy From Temperature Sensors” by Jerry Steele (Electronic Design, August 19, 1996).

Mapping Temperature to Output Voltage or Current

The earliest analog-output temperature sensors developed by National generated output signals that were proportional to absolute temperature (K). The LM135 series has a nominal output voltage equal to 10mV/K, while the LM134 series (a current-output device) produces a current proportional to absolute temperature. The scaling factor is determined by an external resistor.

Because the Celsius and Fahrenheit scales are more convenient in many applications, three of our sensors have output voltages proportional to one of those scales. The LM35 and LM45 produce nominal output voltages equal to 10mV/°C, while the LM34 produces a nominal output equal to 10mV/°F.

While the Celsius and Fahrenheit sensors have more convenient temperature-to-voltage mapping than the absolute temperature sensors, they are somewhat less convenient to use when you need to look at temperatures below 0°C or 0°F. To measure “negative” temperatures with these devices, you need to either provide a negative power supply as in Figure 4.4(a), or bias the sensor above ground and look at the voltage differential between its output and “ground” pins as in Figure 4.4(b).

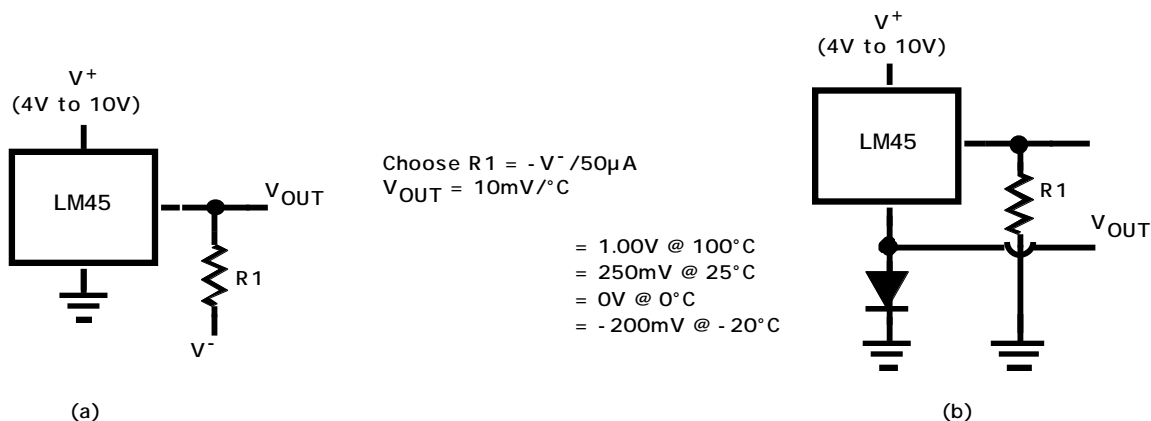


Figure 4.4. Two ways to measure negative temperatures with single-supply sensors. (a) If a negative supply voltage is available, use a pull-down resistor to allow the sensor’s output to go below ground. **(b)** Alternatively, bias the “ground” pin using a diode, a voltage reference, or other voltage source. The differential output voltage will be negative for negative temperatures.



The LM50 and LM60 use an alternative approach. These devices have a built-in positive offset voltage that allows them to produce output voltages corresponding to negative temperatures when operating on a single positive supply. The LM50 has a 10mV/°C scale factor, but the output voltage is 500mV at 0°C. The device is specified for temperatures as low as -40°C (100mV). The LM60's scale factor is 6.25mV/°C, and its output voltage is 424mV at 0°C. The LM60 also is specified for temperatures as low as -40°C (174mV).

Driving Capacitive Loads (These hints apply to analog-output sensors).

National's temperature sensor ICs are micropower circuits, and like most micropower circuits, they generally have a limited ability to drive heavy capacitive loads. The LM34 and LM35, for example, can drive 50 pF without special precautions, while the LM45 can handle 500pF. If heavier capacitive loads are anticipated, it is easy to isolate or decouple the load with a resistor; see Figure 4.5. Note that the series resistor will attenuate the output signal unless the load resistance is very high. If this is a problem, you can improve the tolerance to capacitive loading without increasing output resistance by using a series R-C damper from output to ground as shown in Figure 4.5.


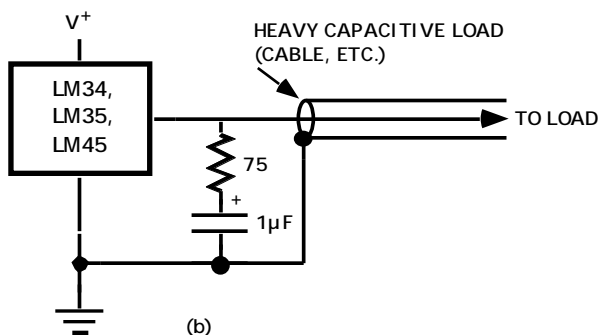


Figure 4.5. Capacitive drive options. The LM34, LM35, and LM45 can drive large external capacitance if isolated from the load capacitance with a resistor as in (a), or compensated with an R-C network as in (b).

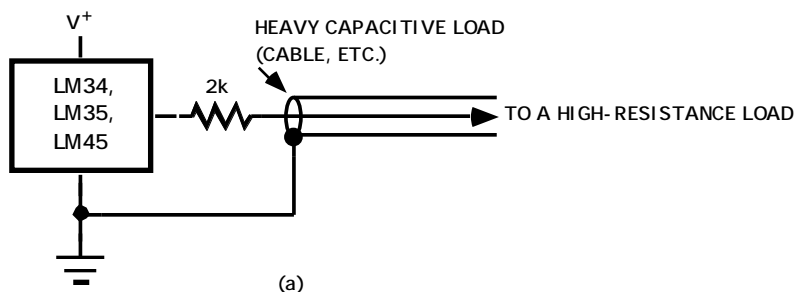

The LM50 and LM60 have internal isolation resistances and can drive any value of capacitance with no stability problems. Ensure that the load impedance is sufficiently high to avoid attenuation of the output signal,

Noise Filtering

Any linear circuit connected to wires in a hostile environment can have its performance adversely affected by intense electromagnetic sources such as relays, radio transmitters, motors with arcing brushes, SCR transients, etc., as its wiring can act as a receiving antenna and its internal junctions can act as rectifiers. In such cases, a $0.1\mu\text{F}$ bypass capacitor from the power supply pin to ground will help clean up power supply noise. Output filtering can be added as well. Sensors like the LM50 and LM60 can drive filter capacitors directly; a $1\mu\text{F}$ to $4.7\mu\text{F}$ output capacitor generally works well. When using sensors that should not directly drive large capacitive loads, you can isolate the filter capacitor with a resistor as shown in Figure 4.5(a), or use the R-C damper in Figure 4.5(b) to provide filtering. Typical damper component values are 75Ω in series with $0.2\mu\text{F}$ to $1\mu\text{F}$.



5. Application Circuits

Personal Computers

Recent generations of personal computers dissipate a lot of power, which means they tend to run hot. The microprocessor and the hard disk drive are notable hot spots. Cooling fans help to keep heat under control, but if a fan fails, or if ventilation paths become blocked by dust or desk clutter, the temperature inside a computer's case can get high enough to dramatically reduce the life of the internal components. Notebook computers, which have no cooling fans, are even more difficult.

High-performance personal computers and servers use monolithic temperature sensors on their motherboards to monitor system temperatures and avert system failure. Typical locations for the sensors are near (sometimes under) the microprocessor, and inside the hard disk drive. In a notebook computer, when the sensor detects excessive temperature, the system can reduce its clock frequency to minimize power dissipation. Fast temperature rise inside a desktop unit or server can indicate fan failure and a well-designed system can notify the user that the unit needs servicing. If temperature continues to rise, the system can shut itself off.

Simple Fan Controller

The circuit in Figure 5.1 senses system temperature and turns a cooling fan on when the sensor's temperature exceeds a preselected value. The LM56 thermostat IC senses temperature and compares its sensor output voltage to the voltages at its V_{T1} and V_{T2} pins, which are set using three external resistors. The 1.25V system voltage reference is internal. As shown, V_{T1} will go low and the fan will turn on when the sensor's temperature exceeds 50°C. If the sensor's temperature rises above 70°C, V_{T2} will go low. This output can be used to slow the system clock (to reduce processor power) or drive an interrupt that causes the microprocessor to initiate a shutdown procedure. If the second output isn't needed, replace the 9.09k resistor with a short, and replace the 2.67k resistor with a 11.8k resistor. V_{T1} will still go low at $T=50^\circ\text{C}$, but V_{T2} will remain inactive.

Typically, the LM56 will be located on the circuit board as close as possible to the microprocessor so that its temperature will be near that of the processor. This circuit is designed for a 12V fan. An alternative approach with a p-channel MOSFET and a 5V fan is shown in Figure 5.2

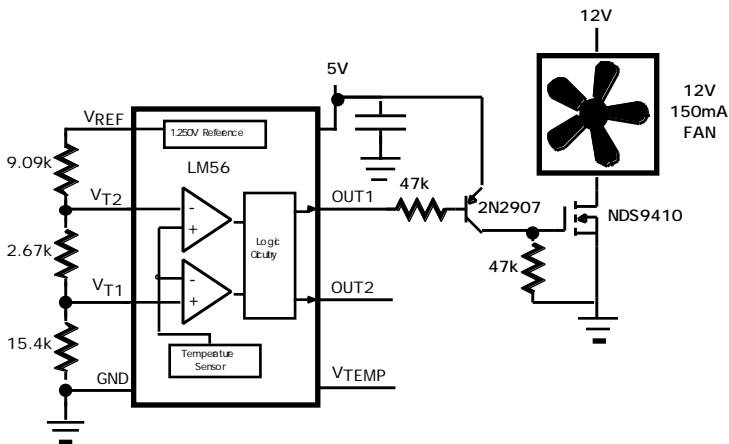


Figure 5.1. This circuit turns on a 12V cooling fan when the LM56's temperature exceeds 50°C. OUT2 goes low when the temperature reaches 70°C. The comparator outputs are open collector, so OUT2 will need a pull-up resistor if it is to drive a logic input.

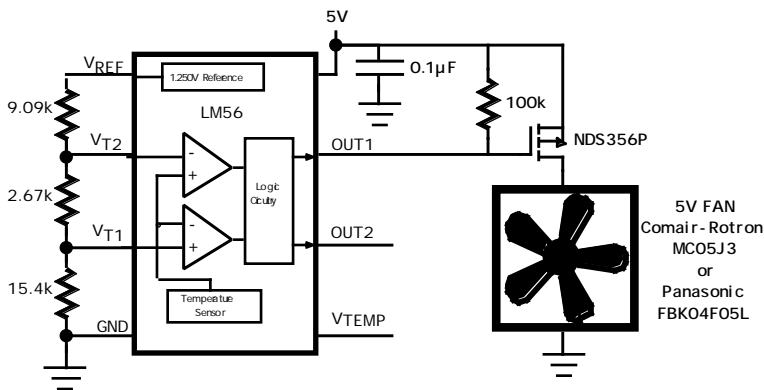


Figure 5.2. This circuit performs the same function as the circuit in 5.1, but it is designed for a 5V cooling fan.

Low/High Fan Controllers

The circuit in Figure 5.3 again uses the LM56, but in this case the fan is always on. When the circuit board's temperature is low, the fan runs at a relatively slow speed. When temperature exceeds 50°C, the fan speed increases to its maximum value. As with the circuits in Figures 5.1 and 5.2, OUT2 is a second logic-level output that indicates that the LM56's temperature is greater than 70°C. Again, if this second logic output is not needed, the V_{REF} and V_{T2} pins can be connected together and the two resistors replaced by a single resistor whose value is equal to the sum of their resistances.



Another variation on this approach uses a MOSFET to turn the fan on at the lower temperature threshold, and the fan's speed control input to increase the fan's speed when the second threshold is exceeded.

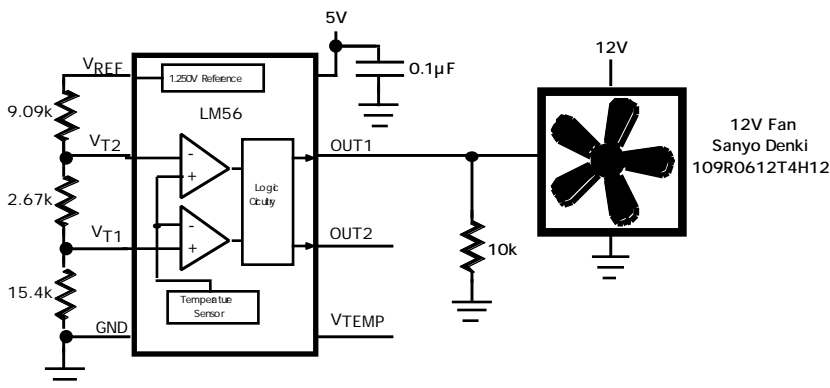


Figure 5.3. You can control some fans without adding a power device to the system. This circuit controls a fan's speed by taking a "third lead" low when temperature is high. This increases the fan's speed to provide additional cooling.

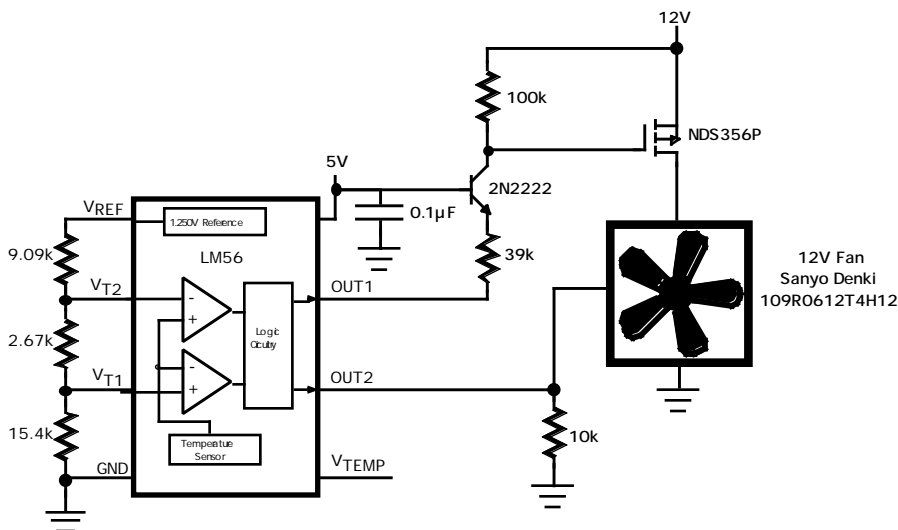


Figure 5.4. By combining the two approaches shown in the previous circuits, you can build a fan controller that turns the fan on at one temperature, then increases its speed if temperature rises above a second threshold.

Digital I/O Temperature Monitor

Temperature sensors with digital I/O are ideally suited to motherboard applications. The LM75 shown here communicates with the host via the I²C bus, which is a 2-wire communications protocol. The LM75 has an internal temperature sensor and delta-sigma ADC, which continuously converts the device's temperature into data. This data can be read at any time over the I²C interface. In addition, the host can program a threshold temperature into the LM75 that will cause the O.S. pin to produce a logic output indicating an



excessive temperature condition. This output can be used to interrupt the processor so that it can take action (such as increasing fan speed, decreasing clock speed, or shutting down the system) to protect the system. For best results, the LM75 should be mounted as close as possible to the microprocessor, either on the motherboard next to the processor, or even under the processor package. In many systems, several LM75s are distributed throughout the chassis to continuously monitor a number of potential hot spots. Up to eight LM75s can be connected to the same I²C bus by selecting eight different addresses with pins A0, A1, and A2.

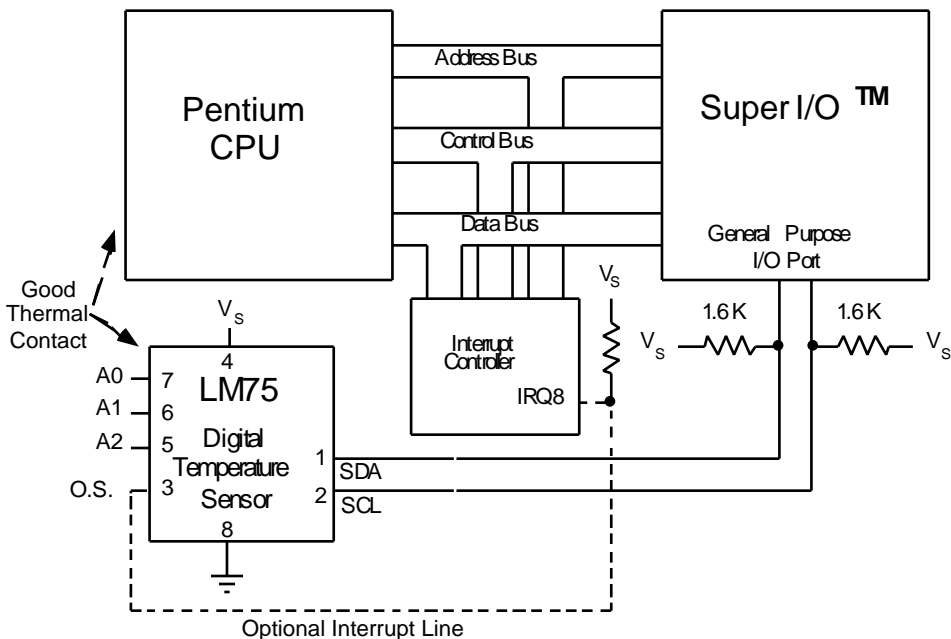


Figure 5.5. Place the LM75 near the microprocessor to monitor the microprocessor's temperature in a motherboard application. Temperature data can be read at any time over the two-wire, I²C compatible serial interface. Up to 8 LM75s can share the same serial bus if their addresses are set to different values using A0, A1, and A2.

Interfacing External Temperature Sensors to PCs

LM75-to-PC interface

The LM75 allows PCs to acquire temperature data through the parallel printer port with minimal circuitry as shown in Figure 5.6. The LM75 gets its power from a line on the parallel printer port. The jumpers on address pins A0, A1, and A2 allow you to select the LM75's address. Up to eight LM75s can be connected to the same port and selected according to the chosen address.

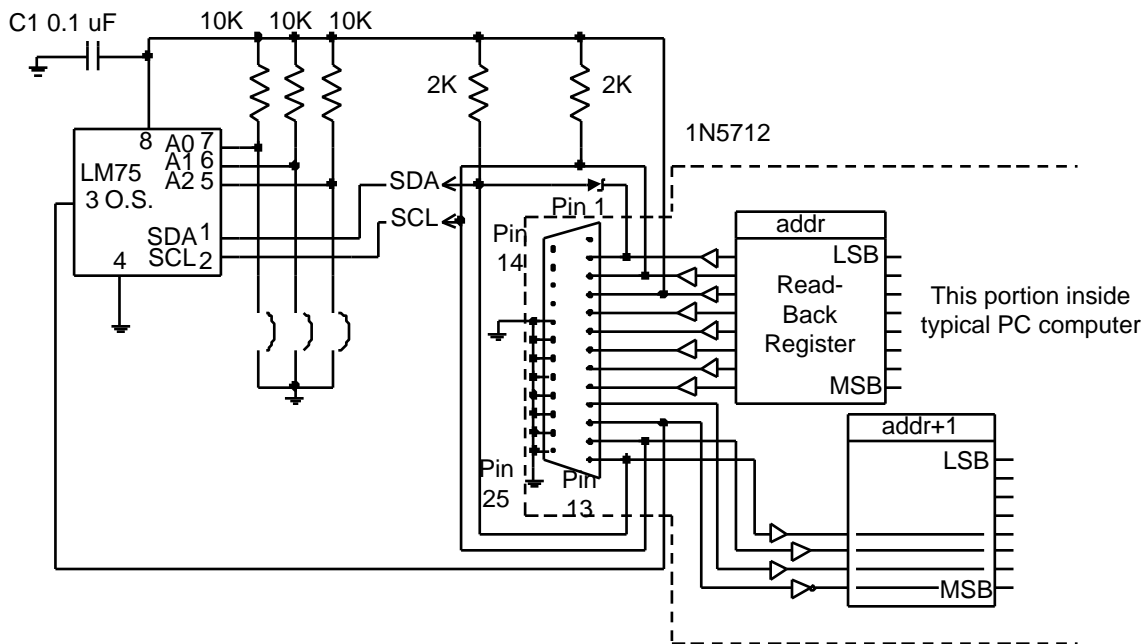


Figure 5.6. PC-Based Temperature Acquisition via the Parallel Printer Port.

Isolated LM75-to-PC

You can couple an LM75 digital output temperature sensor through the isolated I²C interface shown in Figure 5.7. Electrically isolating the sensor allows operation in situations exposed to high common-mode voltages; or could be useful in breaking ground loops. Note that the SCL (clock) line is not bi-directional. The LM75 is a slave, and its SCL pin is an input only.

The O.S. optocoupler is optional and needed only if it is desired to monitor O.S. Provide an isolated supply voltage, either a DC-DC converter or a battery. The LM75 will operate from 3 V to 5 V, and typically requires 250 μ A, while IC1 and IC3 require 7-10 mA each (the LEDs require about 700 μ A, but only when active), for a total current drain of about 30 mA.

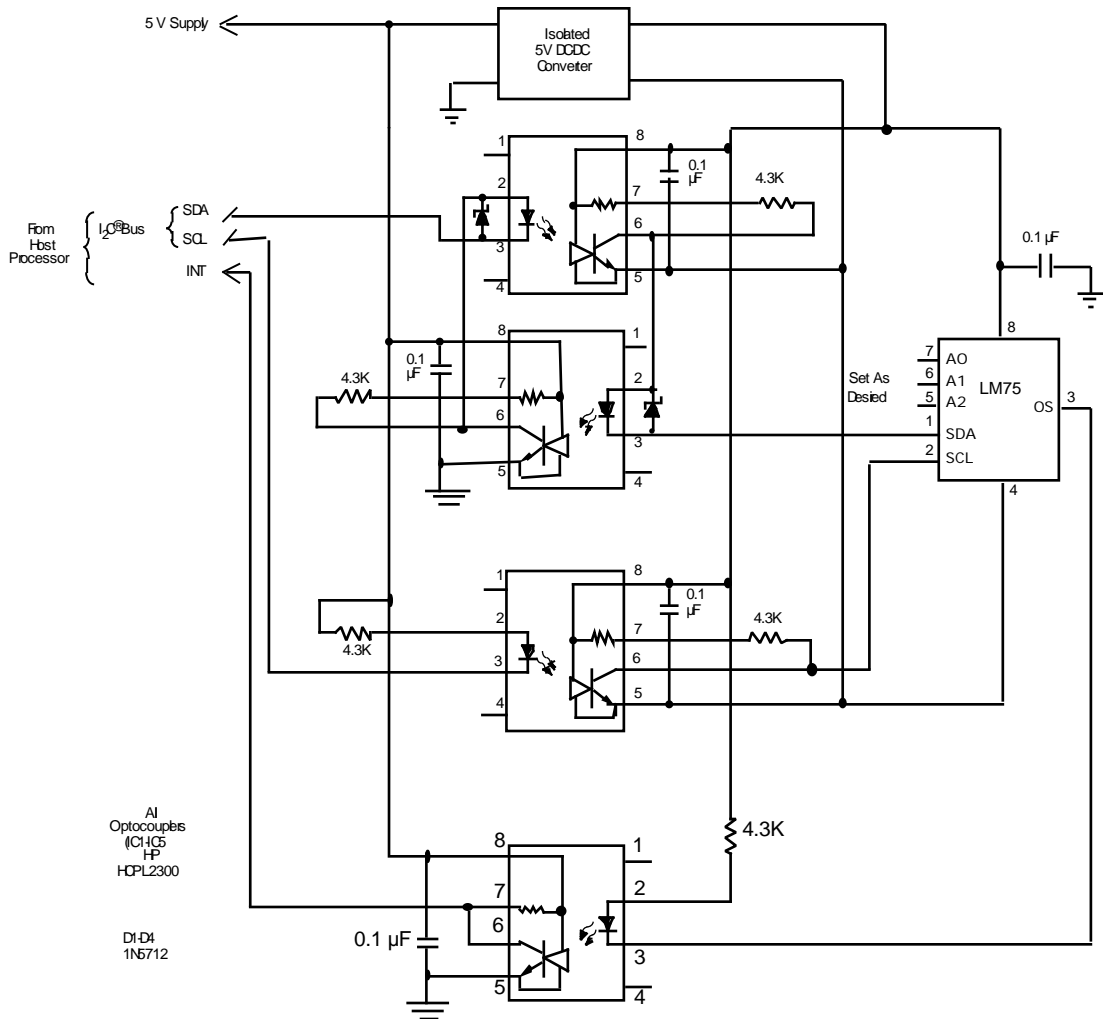


Figure 5.7. Isolated PC-Based Thermometer.

Low-Power Systems

Low-voltage, Low-Power Temperature Sensor with “Shutdown”

Battery-operated portable equipment such as cordless and wireless telephones must operate from very low supply voltages and draw minimal current from the supply in order to maximize battery life. The circuit shown in Figure 5.8 is an LM60 temperature sensor, which has been optimized for portable applications operating from as little as 2.7V. In battery-powered systems, however, even the LM60's low 140μA maximum supply current can hasten the battery discharge if the device is operating full-time. Therefore, the LM60 is shown here being



powered by a CMOS logic gate, which means that the LM60's supply connection serves as the "shutdown" pin. Because temperature changes slowly, and can be measured quickly, the LM60 can be powered up for a small percentage of total operating time, say 1 second every 2 minutes, providing "quick" response to changes in temperature, but using only around $1\mu\text{A}$ average current.


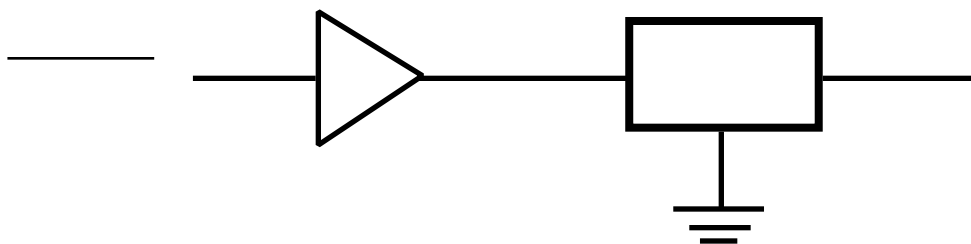


Figure 5.8. 2.7V Temperature Sensor Operating From Logic Gate.


Battery Management

Battery charging circuits range in complexity from simple voltage sources with current-limiting resistors to sophisticated systems based on "smart batteries" that include microcontrollers, temperature sensors, ADCs, and non-volatile memory to store optimum charging data and usage history. A battery's state of charge is usually estimated using terminal voltage and tracking the charge flowing in and out of the cells. Fast chargers for NiCad and NiMH batteries often also rely on cell temperature to help determine when to terminate charging.

In NiCad batteries, charging is an endothermic process, so a NiCad battery pack will either remain at the same temperature or cool slightly during charging. When the battery becomes overcharged, its temperature will begin to rise relatively quickly, indicating that the charging current should be turned off (see Figure 5.9a). Charging is an exothermic process in NiMH batteries, so temperature increases slowly during the entire charge cycle. In either kind of nickel-based battery, both voltage and temperature are often monitored to avoid damage from overcharging. However, in NiMH batteries the change in cell voltage is much slower than in NiCd batteries, so temperature becomes the primary indicator of overcharging.

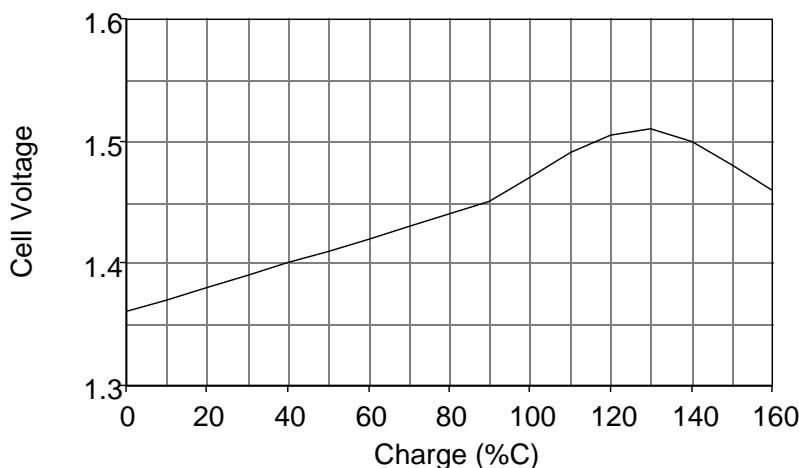

(a)

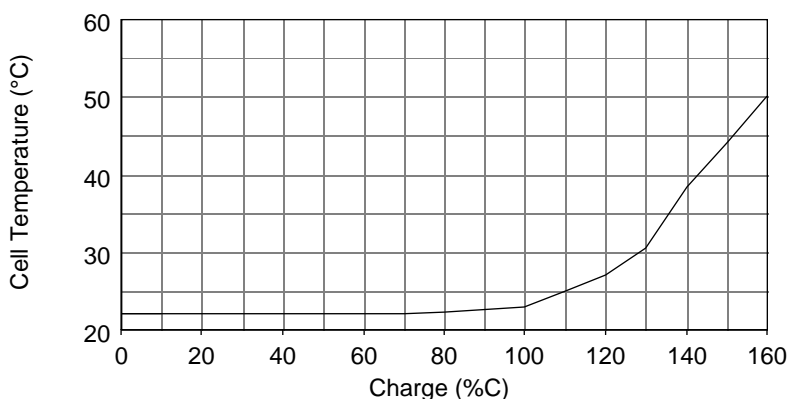

(b)

Figure 5.9. Typical NiCd Fast Charging Curves. Note that both cell voltage and cell temperature provide indication of overcharging.

“No Power” Battery Temperature Monitors

Figure 5.10 shows a temperature sensor housed in a battery pack for charge control and safety enhancement. The LM234 produces an output current that is proportional to absolute temperature ($1\mu\text{A}/^\circ\text{K}$). This current can be converted to a voltage by connecting the LM234’s output to an external resistor, which is located in the host system, or in the battery charger, as shown here. With a 10k resistor, V_{TEMP} is $10\text{mV}/^\circ\text{K}$. By using an external FET to break the current path, current drain by the sensor drops to zero when temperature is not being monitored. Sensor current drain also drops to zero when the battery is unplugged from the charger, or when it is plugged into a charger that has no ac power, thus preventing accidental battery discharge.

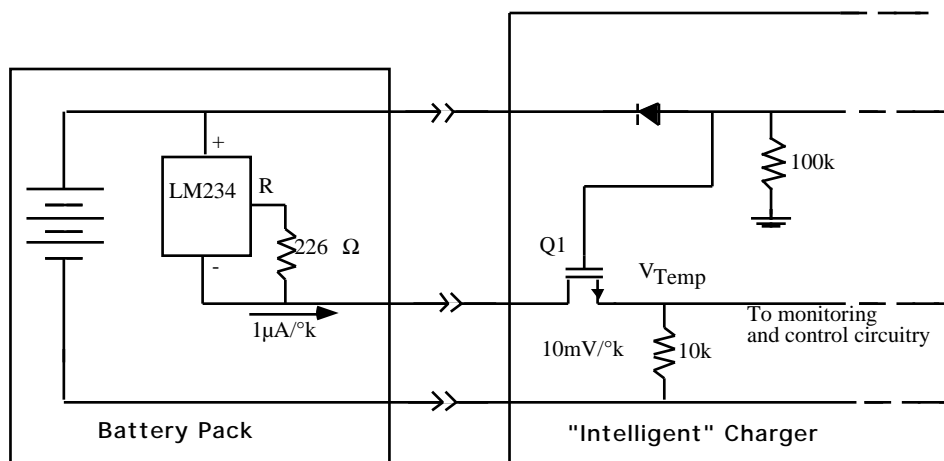


Figure 5.10. This battery pack temperature sensor uses no power unless Q1 (located either in the charger, as shown here, or in the “load system”) is turned on. This helps prevent accidental battery discharge.

Figure 5.11 shows another “no power” battery pack temperature sensor circuit, this one using the LM235 two-terminal temperature sensor. The LM235 behaves like a two-terminal shunt voltage reference with a $10\text{mV}/^\circ\text{K}$ temperature coefficient. A resistor to a positive voltage develops a current to power the LM235. In this circuit, the LM235 is in the battery pack, and the external resistor is in the charger. The LM235 operates at a nominal current of 1mA, and its output voltage (2.98V nominal at 25°C) drives an ADC. The resolution of the ADC depends on the desired sensitivity to temperature changes. With the eight-bit ADC shown here, 1LSB corresponds to 1°C change in temperature. The temperature range for accurate measurements is -23°C to $+125^\circ\text{C}$. If more resolution is needed, a 10-bit converter will have a 1LSB transition every 0.25°C .

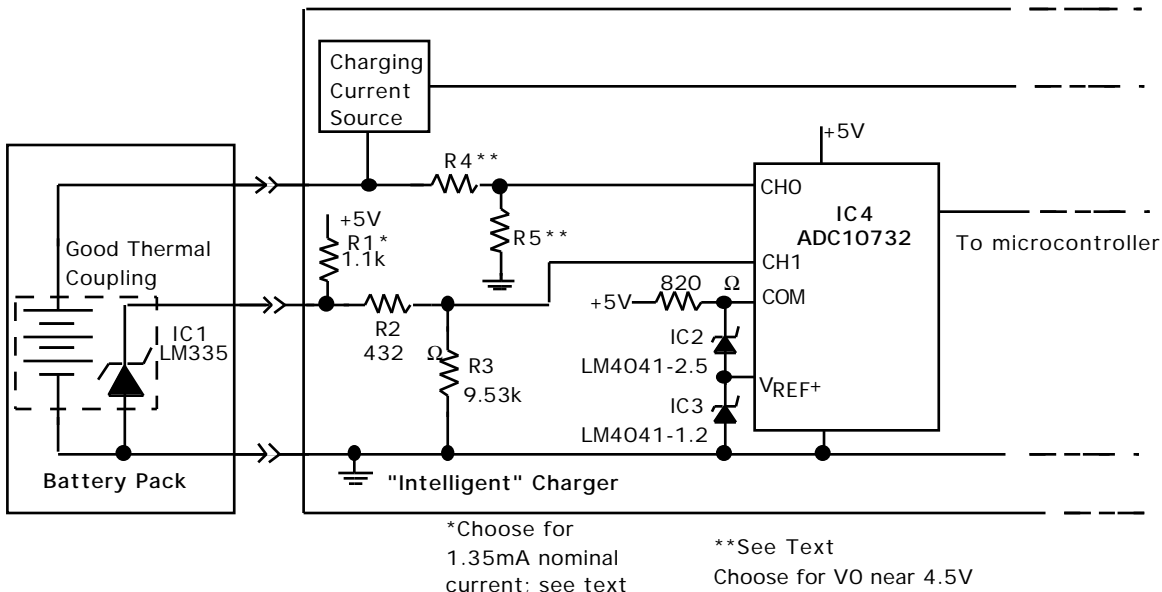


Figure 5.11. Voltage-Output Battery Pack Temperature Sensor

Audio

Audio Power Amplifier Heat sink Temperature Detector and Fan Controller

Figure 5.12 shows an overtemperature detector for power devices. In this example, an audio power amplifier IC is bolted to a heat sink and an LM35 Celsius temperature sensor is either glued to the heat sink near the power amplifier, or mounted on the printed circuit board on the opposite side from the heat sink (if the heat sink is mounted flat against one side of the printed circuit board). The comparator's output goes low if the heat sink temperature rises above a threshold set by R1, R2, and the voltage reference. This fault detection output from the comparator now can be used to turn on a cooling fan. R3 and R4 provide hysteresis to prevent the fan from rapidly cycling on and off. The circuit as shown is designed to turn the fan on when heat sink temperature exceeds about 80°C, and to turn the fan off when the heat sink temperature falls below about 60°C.

A similar circuit is shown in Figure 5.13. In this circuit, the sensor, voltage reference, and comparator are replaced by the LM56. The fan turns on at about 80°C, and the LM56's built-in 5°C hysteresis causes the fan to turn off again when the sensor's temperature drops below about 75°C.

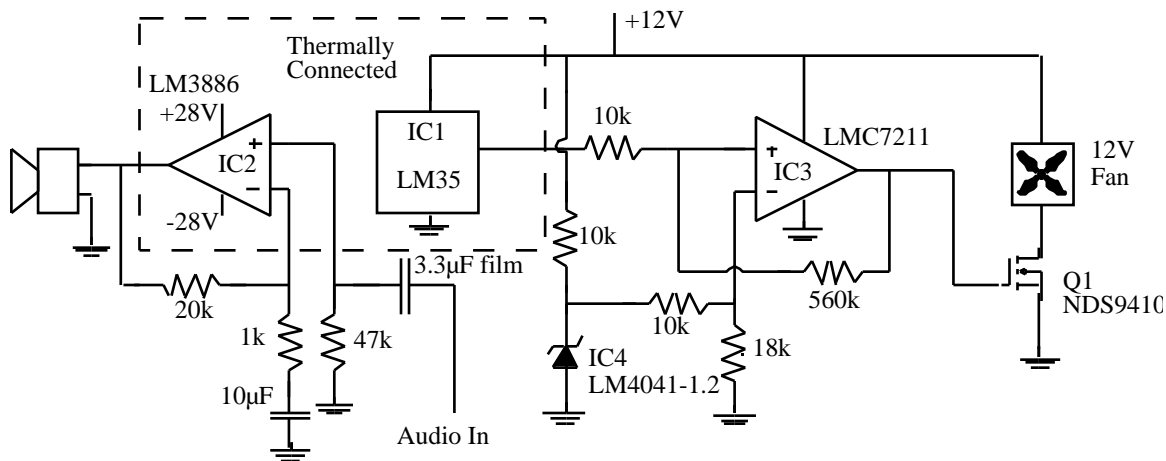


Figure 5.12. In this typical monolithic temperature sensor application, sensor IC1 and its leads are attached to 60W audio power amplifier IC2's heat sink. When the heat sink's temperature rises above the 60°C threshold temperature, comparator IC3's output goes high, turning on the cooling fan.

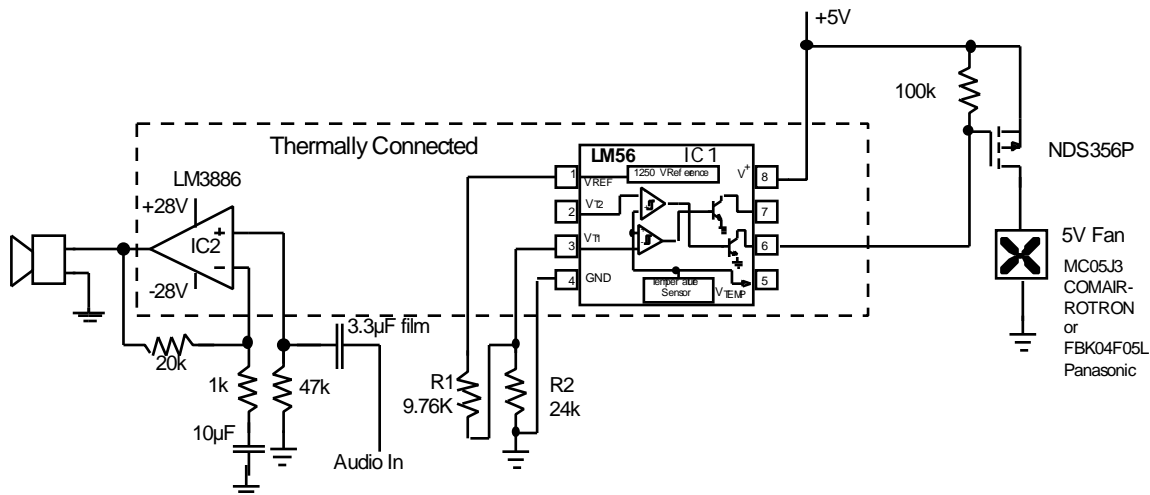


Figure 5.13. This circuit's function is similar to that of the circuit above, except that the sensor, comparator, and voltage reference are integrated within the LM56. In this circuit, the fan turns on at 80°C and off at 75°C.

Other Applications

Two-Wire Temperature Sensor

When sensing temperature in a remote location, it is desirable to minimize the number of wires between the sensor and the main circuit board. A three-terminal sensor needs three wires for power, ground, and output signal; going to two wires means that power and signal must coexist on the same wires. You can use a two-terminal sensor like the LM334 or LM335, but these devices



produce an output signal that is proportional to absolute temperature, which can be inconvenient. If you need an output signal proportional to degrees C, and you must have no more than two wires, the circuit in Figure 5.14 may be a good solution. The sensor's output voltage is dc, and power is transmitted as an ac signal.

The ac power source for the sensor is a sine-wave oscillator (A1 and A2) coupled to the two-wire line through blocking capacitor C6. At the LM45 sensor, D1, D2, C1, and C3 comprise a half-wave voltage-doubler rectifier that provides power for the sensor. R2 isolates the sensor's output from the load capacitance, and L1 couples the output signal to the line. L1 and C2 protect the sensor's output from the ac on the two-wire line.

At the output end of the line, R3, L2, and C2 form a low-pass filter to remove ac from the output signal. C5 prevents dc current from flowing in R3, which would attenuate the temperature signal. The output should drive a high-impedance load (preferably 100kΩ or greater).

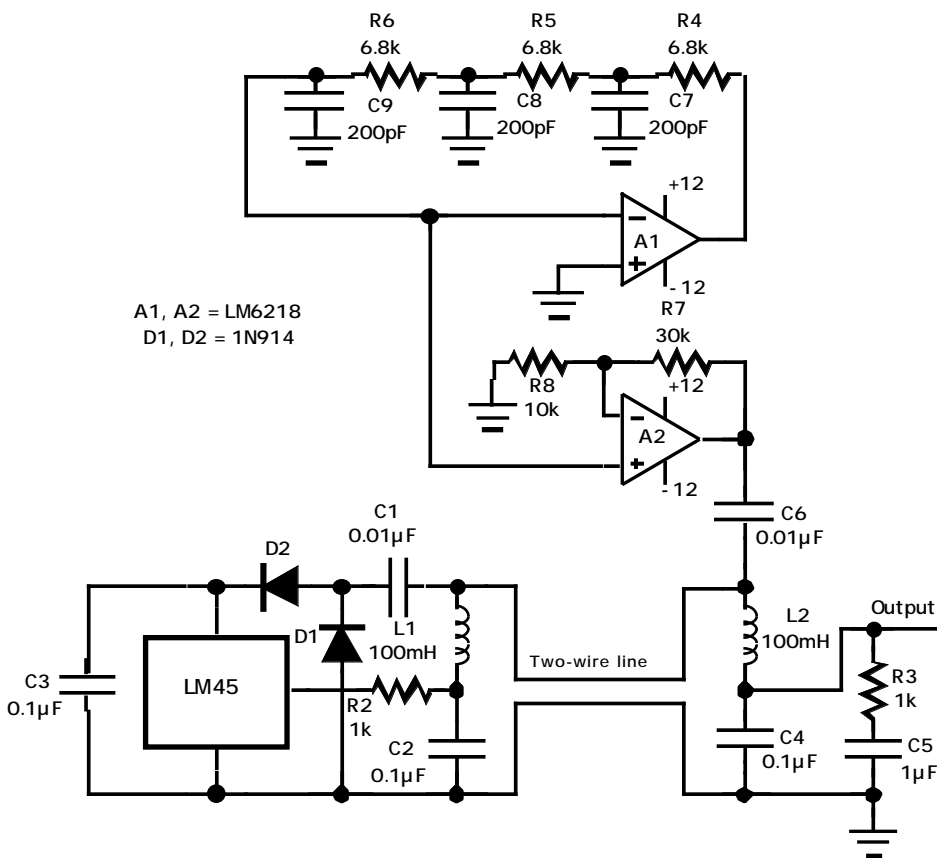


Figure 5.14. This two-wire remote temperature sensor transmits the dc output of the sensor without reducing its accuracy.



4-to-20mA Current Transmitter (0°C to 100°C)

This circuit uses an LM45 or LM35 temperature sensor to develop a 4-to-20mA current. The temperature sensor's output drive is augmented by a PNP to drive a 62.5Ω load; this provides the 160μA/°C transfer function slope required to develop a 4-to-20mA output current for a 0°C to 100°C temperature range. The LM317 voltage regulator and its load resistors draw about 2.8mA from the supply. The remaining 1.2mA is obtained by adjusting the 50Ω potentiometer to develop an offset voltage on the temperature sensor's ground pin.

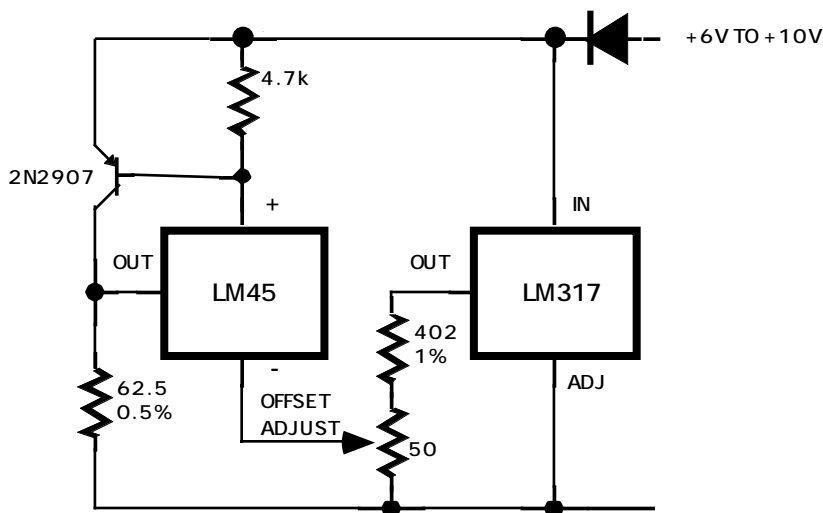


Figure 5.15. 4-20mA Current Transmitter Temperature Sensor

Multi-Channel Temperature-to-Digital Converter

This circuit implements a low-cost system for measuring temperature at several points within a system and converting the temperature readings to digital form. With the components shown here, up to 19 LM45 temperature sensors drive separate inputs of an ADC08019 8-bit, 19-channel ADC with serial (microwire, SPI) data interface. The tiny SOT-23 sensor packages allow the designer to place the sensors in virtually any location within the system.

The 1.28V reference voltage is chosen to provide a conversion scale of 1LSB=5mV=0.5°C, with full-scale equal to 128°C. The R-C network at the sensors' outputs provide protection against oscillation if capacitive loads (or cables) may be encountered, and also help filter output noise. The reference voltage can be manually adjusted to 1.28V with the 10k potentiometer, or the potentiometer can be replaced with a fixed resistor. If 5% values will be used, a 3.3kΩ resistor will work. For better accuracy, use 1% resistors; the pot can then be replaced by a 3.24kΩ resistor.

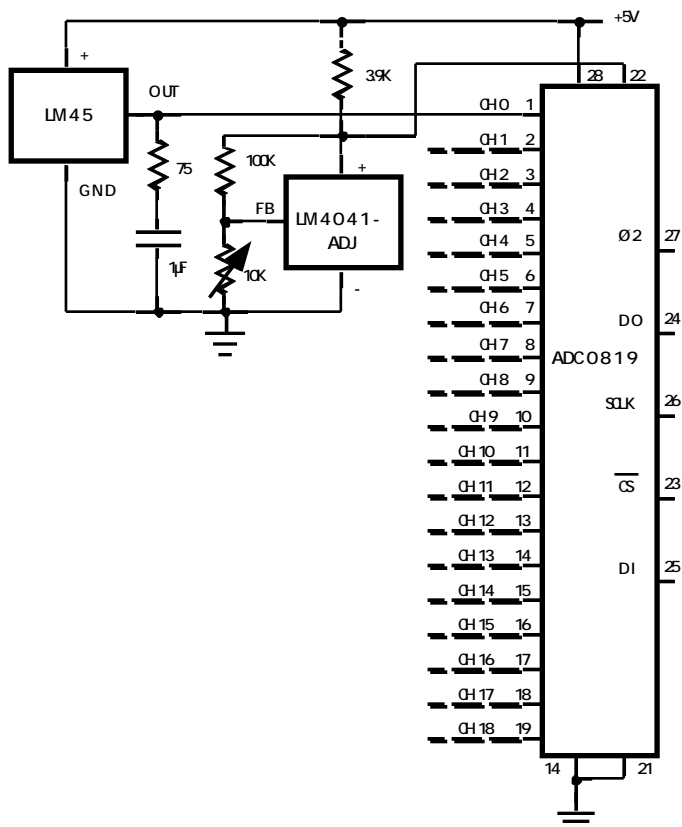


Figure 5.16. 19-Channel Temperature-to-Digital Converter. Only one LM45 temperature sensor is shown. One LM45 can be connected to each of the ADC0819's 19 inputs.

Oven Temperature Controllers

The circuit in Figure 5.17 operates on a single +5V supply and controls the temperature of an oven. As shown, the circuit keeps the oven temperature at 75°C, which is ideal for most types of quartz crystals.

The inverting input of amplifier A1 (1/2 of an LM392 amplifier/comparator dual) comes from the LM335 temperature sensor, which should be in good thermal contact with the heater, and the non-inverting input is the output of a voltage divider from the LM4040-4.1 voltage reference. With the divider components shown, the non-inverting input is at 3.48V, which is equal to the LM335's output at 75°C. The amplifier has a gain of 100 to the difference between the measured temperature and the set-point.

The output of A1 modulates the duty cycle of the oscillator built around comparator C1. When the oven is cold, the output of A1 is high, which charges the capacitor and forces C1's output low. This turns on Q1 and delivers full dc power to the heater. As the oven temperature approaches the set-point, A1's



output goes lower, and adjusts the oscillator's duty cycle to servo the oven temperature near the set-point.

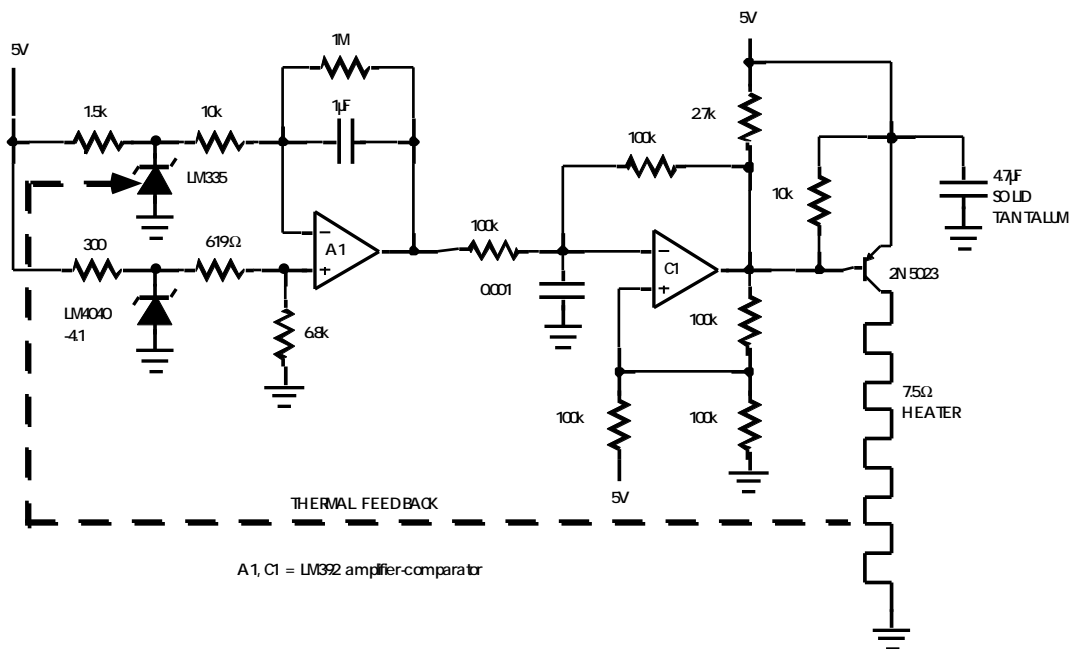


Figure 5.17. 5V Oven Controller

Isolated Temperature-to-Frequency Converter

A simple way to transmit analog information across an isolation barrier is to first convert the analog signal into a frequency. The frequency can then easily be counted on the other side of the isolation barrier by a microcontroller. Figure 5.18 shows a simple way of implementing this. The LM45's analog output, which is proportional to temperature, drives the input of an LM131 configured as a V-F converter. Over the temperature range of 2.5°C to 100°C, the LM45 produces output voltages from 25mV to 1V, which causes the LM131 to develop output frequencies from 25Hz to 1kHz.

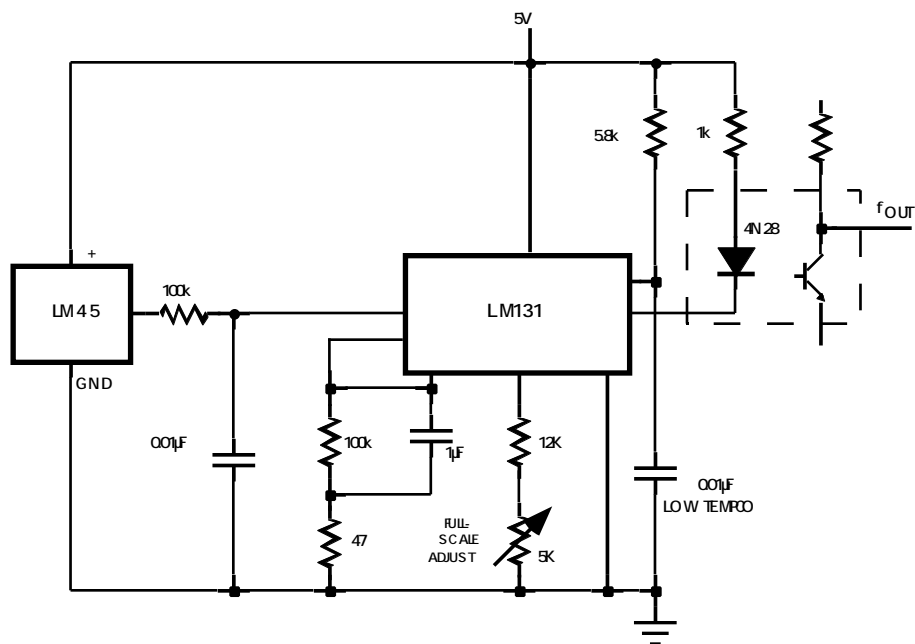


Figure 5.18. Isolated Temperature-to-Frequency Converter